

## LAB4 - 2 digit counter using 2 seven-seg-displays

Group A :


- Jihun Choi(Bronco ID#: 011841206)
- Jacky Li(Bronco ID#:014181245)

Prof.Aly

ECE3300L.02 - Summer 2022

This lab4 is about designing a 2 digit counter (0~99) using 2 seven-seg-displays by instantiation using vivado software and test the results with FPGA board.

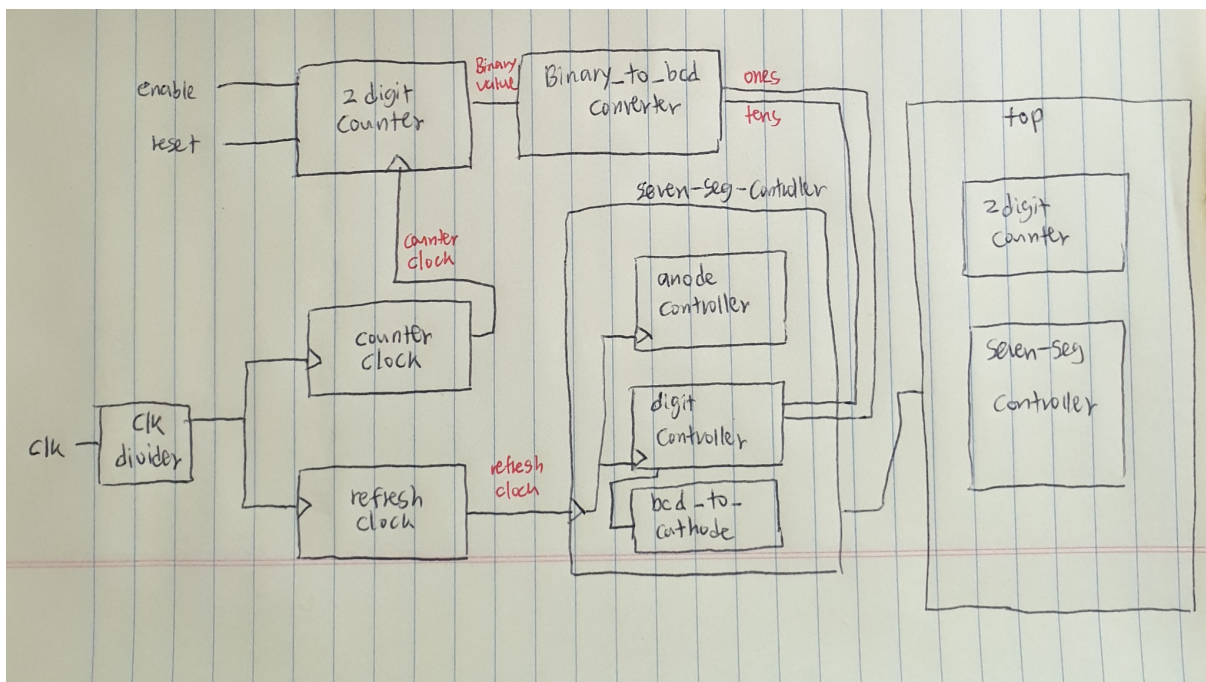reference: <https://www.youtube.com/watch?v=s4IPOQ1VAkU&t=362s>



1) we create clock\_divider module to divide clock for seven segment display

(input clk, output divided\_clk)

2) we create refreshcounter module to have separate counter to be used in anode controller and digit controller

(input refresh\_clock, output refreshcounter)

3) we create anode\_controller module to control which 7 sevenment to be turned on by using refreshcounter

(input refreshcounter, output [7:0] AN since there are 8 seven seg available, but we are only using 2)

4) we create digit\_controller module to control which locations of digit(one's or ten's) to show by using refreshercounter

(input refreshcounter, [3:0] ones, [3:0] tens, output [3:0] digit )

5) we create binary\_to\_bcd\_converter module to convert binary number to bcd format using idea of shift

(input [7:0] number, output [3:0] ones, output [3:0] tens)

refrence:

[https://www.google.com/search?q=binary+to+bcd+shift+add+3&rlz=1C1CHZN\\_koKR958KR958&oq=&aqs=chrome.3.69i59i450l8.43413477j0j15&sourceid=chrome&ie=UTF-8#kpvalbx=MATAYp-fNKDVkPIPiLybOA16](https://www.google.com/search?q=binary+to+bcd+shift+add+3&rlz=1C1CHZN_koKR958KR958&oq=&aqs=chrome.3.69i59i450l8.43413477j0j15&sourceid=chrome&ie=UTF-8#kpvalbx=MATAYp-fNKDVkPIPiLybOA16)

6) we create bcd\_to\_cathode module to connect bcd number (0~9) to corresponding cathode for seven segment display

(input [3:0] digit, output reg [6:0] cathode)

7) we create two\_digit\_counter module to write function of the main idea (reset and enable to pause)

(input clk, enable, reset , output [7:0] counter)

8) we create seven\_seg\_controller to connect refresh counter module to anode\_controller and digit\_controller.

Then, connect digit\_controller with bcd\_to\_cathode

(input refresh\_clock, input [3:0] ones, tens, output [7:0] AN, output [6:0] cathode)

9) we create top module to connect two\_digit\_counter to be connected with other modules

10) we create a top.xdc file and connect the correct ports.

11) we performed the simulation,

```
module top_tb();


    reg clk = 0;
    reg enable = 0;
    reg reset = 0;
    wire [7:0] AN;
    wire [6:0] cathode;
    wire DP=1;

    top top1(
        .clk(clk),
        .enable(enable),
        .reset(reset),
        .AN(AN),
        .cathode(cathode),
        .DP(DP)
    );

    always #5 clk = ~clk;
    initial
        begin
            #500
                enable = 1;
        end

endmodule
```

---

 

Simulation video was not included in the demo video, since the laptop that was testing the simulation was not able to handle for running it for 1 seconds. So, only a screen shot was provided.


Video link:

<https://youtu.be/2OLKznhubEw>


or

<https://drive.google.com/file/d/1CL9M76JCyxCSSrKhnl69roycP3X1VjHo/view?usp=sharing>

Elaborated Design:

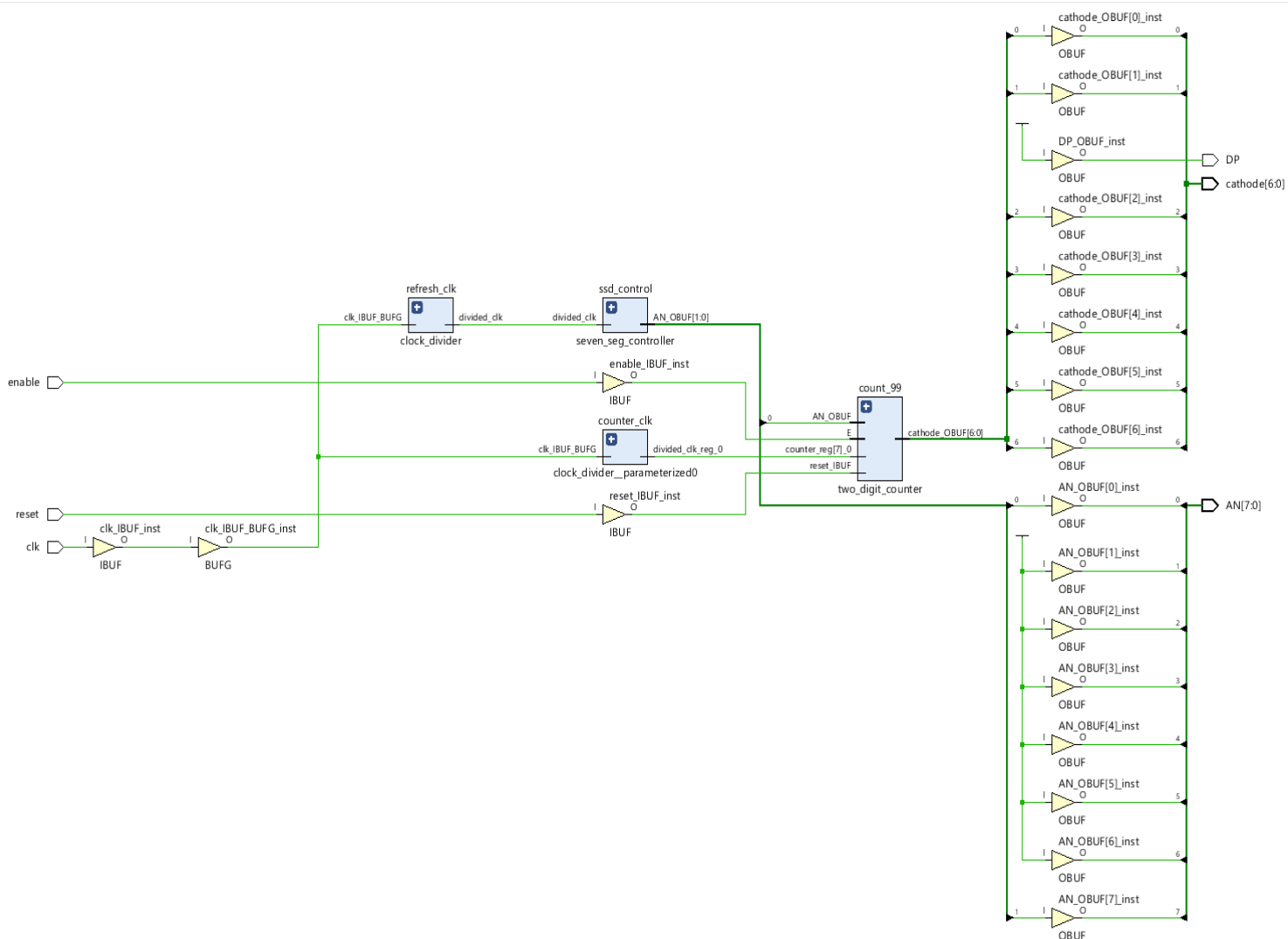

Utilization:

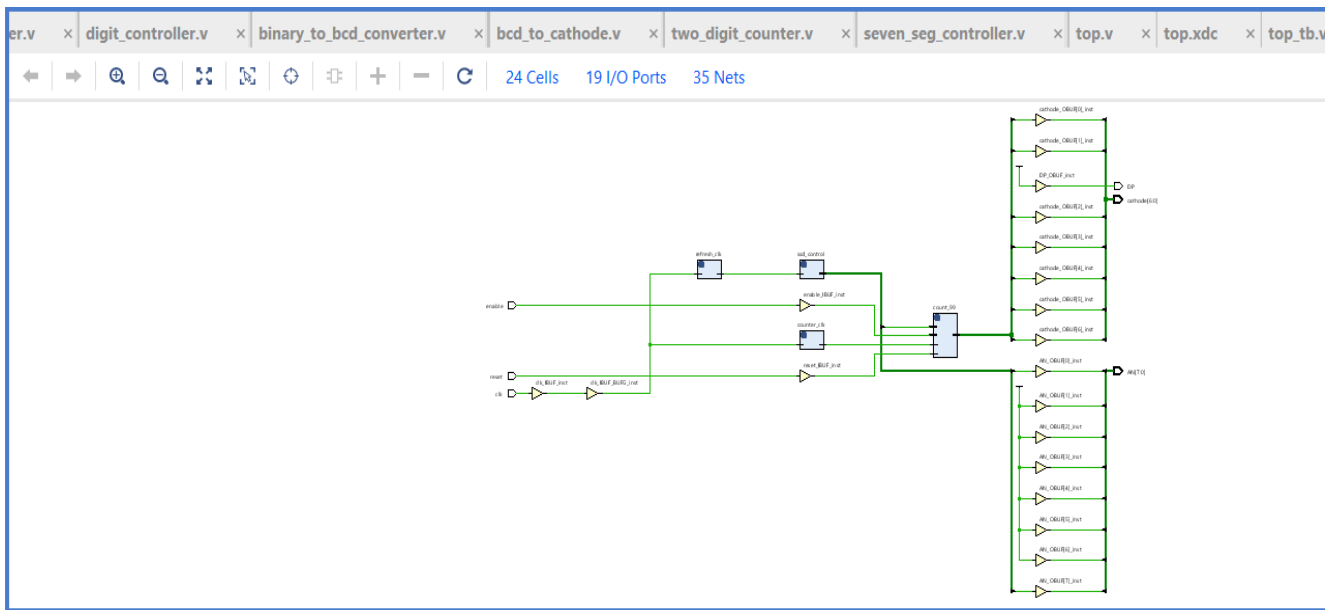

Tcl Console	Messages	Log	Reports	Design Runs	Power	DRC	Methodology	Timing	Utilization	x																																										
Hierarchy																																																				
<table><tr><th>Name</th><th>Slice LUTs (63400)</th><th>Slice Registers (126800)</th><th>Slice (15850)</th><th>LUT as Logic (63400)</th><th>Bonded IOB (210)</th><th>BUFGCTRL (32)</th></tr><tr><td>top</td><td>43</td><td>75</td><td>38</td><td>43</td><td>19</td><td>1</td></tr><tr><td>count_99 (two_digit_counter)</td><td>22</td><td>8</td><td>8</td><td>22</td><td>0</td><td>0</td></tr><tr><td>counter_clk (clock_divider__parameterized0)</td><td>10</td><td>33</td><td>16</td><td>10</td><td>0</td><td>0</td></tr><tr><td>refresh_clk (clock_divider)</td><td>10</td><td>33</td><td>16</td><td>10</td><td>0</td><td>0</td></tr><tr><td>ssd_control (seven_seg_controller)</td><td>1</td><td>1</td><td>2</td><td>1</td><td>0</td><td>0</td></tr></table>											Name	Slice LUTs (63400)	Slice Registers (126800)	Slice (15850)	LUT as Logic (63400)	Bonded IOB (210)	BUFGCTRL (32)	top	43	75	38	43	19	1	count_99 (two_digit_counter)	22	8	8	22	0	0	counter_clk (clock_divider__parameterized0)	10	33	16	10	0	0	refresh_clk (clock_divider)	10	33	16	10	0	0	ssd_control (seven_seg_controller)	1	1	2	1	0	0
Name	Slice LUTs (63400)	Slice Registers (126800)	Slice (15850)	LUT as Logic (63400)	Bonded IOB (210)	BUFGCTRL (32)																																														
top	43	75	38	43	19	1																																														
count_99 (two_digit_counter)	22	8	8	22	0	0																																														
counter_clk (clock_divider__parameterized0)	10	33	16	10	0	0																																														
refresh_clk (clock_divider)	10	33	16	10	0	0																																														
ssd_control (seven_seg_controller)	1	1	2	1	0	0																																														

Power report:

Settings

Summary (0.124 W, Margin: N/A)

Power Supply

Utilization Details

- Hierarchical (0.027 W)
- Clocks (0.001 W)
- Signals (0.001 W)
  - Data (0.001 W)
  - Clock Enable (<0.001 W)
  - Set/Reset (<0.001 W)
- Logic (<0.001 W)
- I/O (0.025 W)

Power analysis from Implemented netlist. Activity derived from constraints files, simulation files or vectorless analysis.

Total On-Chip Power:0.124 W

Design Power Budget:Not Specified

Power Budget Margin:N/A

Junction Temperature:25.6°C

Thermal Margin:59.4°C (12.9 W)

Effective  $\theta$ JA:4.6°C/W

Power supplied to off-chip devices: 0 W

Confidence level:Medium

[Launch Power Constraint Advisor](#) to find and fix invalid switching activity

On-Chip Power

22%

78%

Dynamic:0.027 W (22%)

Clocks:0.001 W (4%)

Signals:0.001 W (2%)

Logic:<0.001 W (1%)

I/O:0.025 W (93%)

Device Static:0.097 W (78%)